


Messina, 20 December 2021

Exercise 1

Solve the given circuit below by using the node analysis and D as a reference node (A, B and C are the nodes 1, 2 and 3).

a) Write the G matrix in analytical form.

b) Compute the value of the voltage at the node A, B and C, using the following values for $R_1 = 1 \Omega$, $R_2 = 2 \Omega$, $R_3 = 10 \Omega$, $R_4 = 2 \Omega$, $I_1 = 2 \text{ A}$, and $\alpha = 2$;

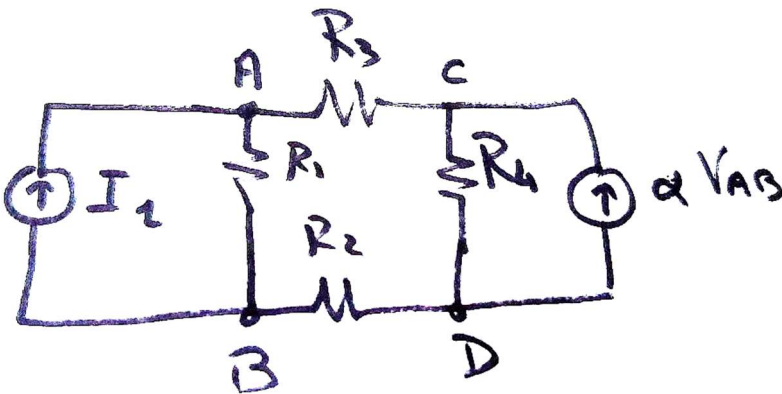

Exercise 2


Solve the given circuit below.

a) Compute analytically the Thevenin Equivalent circuit from node A considering the positive node of the voltage Thevenin generator toward the node A.

b) Compute V_0 analytically.

c) Compute the value of V_0 considering the following parameters $R_1 = 5 \Omega$, $R_2 = 1 \Omega$, $R_3 = 5 \Omega$, $R_4 = 2 \Omega$, $R_5 = 4 \Omega$, $R_6 = 1 \Omega$, $I_1 = 5 \text{ A}$, $E_1 = 2 \text{ V}$ and $E_2 = 4 \text{ V}$.

d) Compute the value of I_4 considering the same values for the device reported in point c).

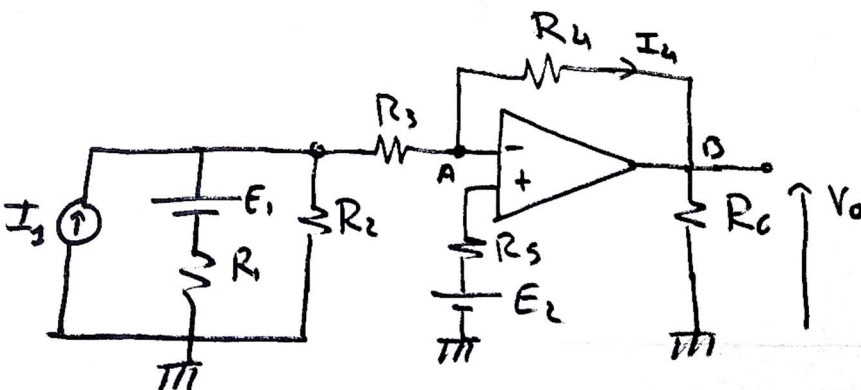

Exercise 3

Draw the circuit which can solve the following differential equation: $\frac{d^2 v_0}{dt^2} = -4 \frac{dv_0}{dt} - 3v_0 + 2 \sin(10t)$. The initial conditions are set to zero, use R and C in order that the product $RC=1 \text{ s}$. Do not assign values to R and/or C.

Sign here _____

Exercise 1:

a)

b)

Exercise 2:

a)

b)

c)

d)

Exercise 3:

Solution 1

a)

$$\begin{pmatrix} G_1 + G_3 & -G_1 & -G_3 \\ -G_1 & G_1 + G_2 & 0 \\ -G_3 & 0 & G_3 + G_4 \end{pmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix} = \begin{pmatrix} I_1 \\ -I_1 \\ \alpha V_A - \alpha V_B \end{pmatrix} \rightarrow \begin{pmatrix} G_1 + G_3 & -G_1 & -G_3 \\ -G_1 & G_1 + G_2 & 0 \\ -G_3 - \alpha & +\alpha & G_3 + G_4 \end{pmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix} = \begin{pmatrix} I_1 \\ -I_1 \\ 0 \end{pmatrix}$$

b) $V_A = 3.6364 \text{ V}$; $V_B = 1.0909 \text{ V}$; $V_C = 9.0909 \text{ V}$

Solution 2

$$E_{TH} = \frac{I_1 + E_1 / R_1}{1 / R_1 + 1 / R_2}$$

a)

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} + R_3$$

b) V_0 is given by two contributions. Applying the superposition principle, one is from the inverting amplifier and one from non-inverting amplifier.

$$V_0 = -E_{TH} \frac{R_4}{R_{TH}} + E_2 \left(1 + \frac{R_4}{R_{TH}}\right)$$

c) $V_0 = 3.8 \text{ V}$

$$d) I_4 = \frac{V_A - V_0}{R_4} = \frac{E_2 - V_0}{R_4} = 0.08 \text{ A}$$

Solution 3

