


Messina, 10 January 2022

**Exercise 1**

Solve the given circuit below by using the node analysis and D as a reference node (A, B and C are the nodes 1, 2 and 3).

a) Write the G matrix in analytical form.

b) Compute the value of the voltage at the node A, B and C, using the following values for  $R_1 = 2 \Omega$ ,  $R_2 = 6 \Omega$ ,  $R_3 = 4 \Omega$ ,  $I_1 = 4 \text{ A}$ ,  $I_2 = 1 \text{ A}$ , and  $\alpha = -1$ ;

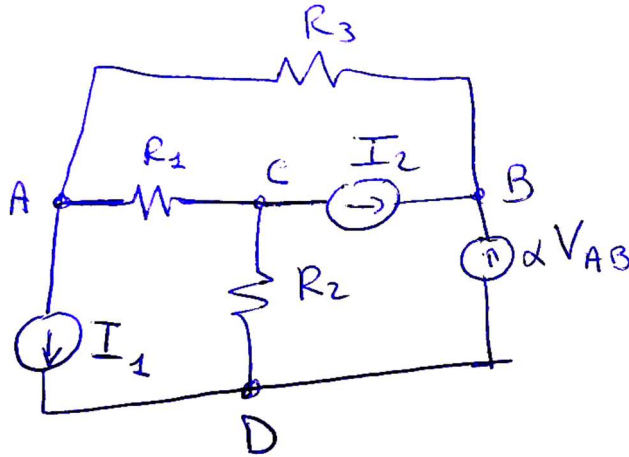

**Exercise 2**


Solve the given circuit below.

a) Compute analytically the Thevenin Equivalent circuit from node A considering the positive node of the voltage Thevenin generator toward the node A.

b) Compute  $V_0$  analytically.

c) Compute the value of  $V_0$  considering the following parameters  $R_1 = 2 \Omega$ ,  $R_2 = 4 \Omega$ ,  $R_3 = 3 \Omega$ ,  $R_4 = 2 \Omega$ ,  $R_5 = 5 \Omega$ ,  $R_6 = 10 \Omega$ ,  $R_7 = 100 \Omega$ ,  $I_1 = 4 \text{ A}$ , and  $E_1 = 4 \text{ V}$ .

d) Compute the value of  $V_+$  considering the same values for the devices as reported in the point c).

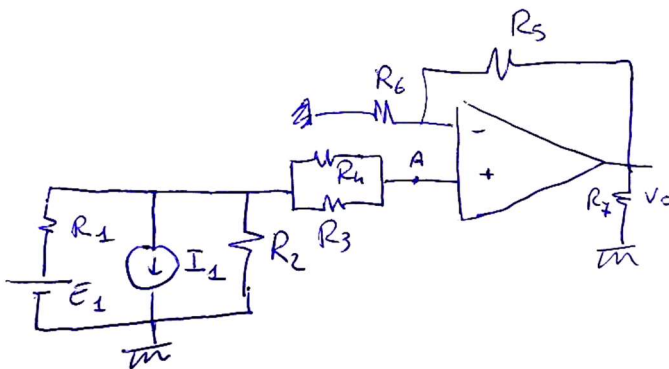

**Exercise 3**

Draw the circuit which can solve the following differential equation:  $\frac{1}{2} \frac{d^2 v_0}{dt^2} = -\frac{4}{3} \frac{dv_0}{dt} - v_0 + 6 \cos(10t)$ . The initial conditions are set to zero, use R and C in order that the product  $RC=1 \text{ s}$ . Do not assign values to R and/or C.

Sign here \_\_\_\_\_

Exercise 1:

a)

b)

Exercise 2:

a)

b)

c)

d)

Exercise 3:

**Solution 1**

a)

$$\begin{pmatrix} G_1 + G_3 & -G_3 & -G_1 \\ -G_3 & G_3 & 0 \\ -G_1 & 0 & G_1 + G_2 \end{pmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix} = \begin{pmatrix} -I_1 \\ I_2 + \alpha V_A - \alpha V_B \\ -I_2 \end{pmatrix} \rightarrow \begin{pmatrix} G_1 + G_3 & -G_3 & -G_1 \\ -G_3 - \alpha & G_3 + \alpha & 0 \\ -G_1 & 0 & G_1 + G_2 \end{pmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix} = \begin{pmatrix} -I_1 \\ I_2 \\ -I_2 \end{pmatrix}$$

b)  $V_A = -40.67 \text{ V}$ ;  $V_B = -42 \text{ V}$ ;  $V_C = -32 \text{ V}$

**Solution 2**

$$E_{TH} = \frac{-I_1 + E_1 / R_1}{1 / R_1 + 1 / R_2}$$

a)

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4}$$

b) This is a non-inverting amplifier.  $V_0$  is given by

$$V_0 = E_{TH} \left( 1 + \frac{R_5}{R_6} \right)$$

c)  $V_0 = -4 \text{ V}$

d)  $V_+ = E_{TH} = -2.667 \text{ V}$

**Solution 3**

We rewrote the equation as

$$\frac{d^2 v_0}{dt^2} = -\frac{8}{3} \frac{dv_0}{dt} - 2v_0 + 12 \cos(10t)$$

