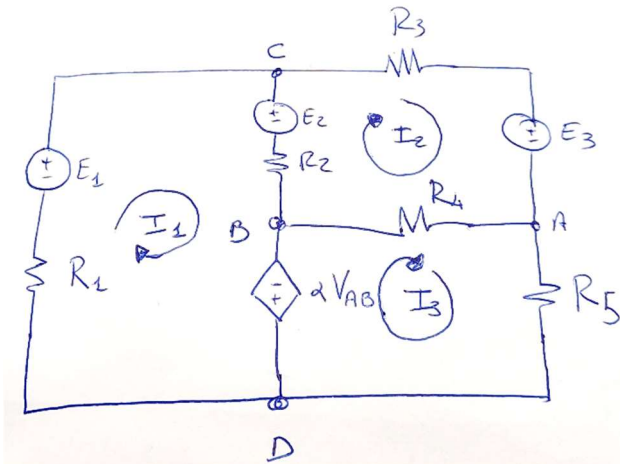


Messina, 22 February 2022

Exercise 1

Solve the given circuit below by using the mesh analysis for the three currents as indicated.


- a) Write the R matrix in analytical form.
- b) Compute the value of the mesh currents I_1 , I_2 and I_3 , using the following values for $R_1 = 4 \Omega$, $R_2 = 6 \Omega$, $R_3 = 4 \Omega$, $R_4 = 8 \Omega$, $R_5 = 4 \Omega$, $E_1 = 2 \text{ V}$, $E_2 = -5 \text{ V}$, $E_3 = 4 \text{ V}$, and $\alpha = 2$;



Exercise 2

Solve the given circuit below.

- a) Compute analytically the expression of the V_0 as a function of I_1 and E_1 .
- b) Compute the value of V_0 considering the following parameters $R_1 = 2 \Omega$, $R_2 = 1 \Omega$, $R_3 = 10 \Omega$, $R_4 = 5 \Omega$, $R_5 = 3 \Omega$, $I_1 = 2 \text{ A}$, and $E_1 = 14 \text{ V}$.
- c) Compute the value of I_{R5} considering the same values for the devices as reported in the point b).

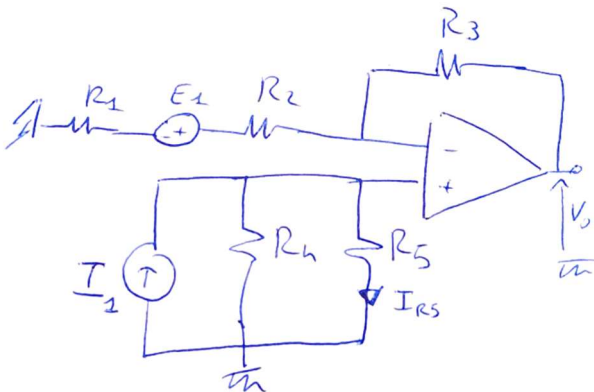

Exercise 3

For a given an RC circuit with $R=1\Omega$ and $C=0.1 \text{ F}$. Compute the voltage of across the Capacitor after 200 ms $v_C(200 \text{ ms})$ considering that the voltage at $t=0\text{s}$ across the Capacitor equal to 1V ($v_C(0)=1\text{V}$).

Sign here _____

Exercise 1:

a)

b)

Exercise 2:

a)

b)

c)

Exercise 3:

Solution 1

a)

$$\begin{pmatrix} R_1 + R_2 & -R_2 & 0 \\ -R_2 & R_2 + R_3 + R_4 & -R_4 \\ 0 & -R_4 & R_4 + R_5 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} E_1 - E_2 + \alpha V_{AB} \\ E_2 - E_3 \\ -\alpha V_{AB} \end{pmatrix}$$

$$V_{AB} = R_4 I_2 - R_4 I_3$$

$$\begin{pmatrix} R_1 + R_2 & -R_2 & 0 \\ -R_2 & R_2 + R_3 + R_4 & -R_4 \\ 0 & -R_4 & R_4 + R_5 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} E_1 - E_2 + \alpha R_4 I_2 - \alpha R_4 I_3 \\ E_2 - E_3 \\ -\alpha R_4 I_2 + \alpha R_4 I_3 \end{pmatrix}$$

$$\begin{pmatrix} R_1 + R_2 & -R_2 - \alpha R_4 & \alpha R_4 \\ -R_2 & R_2 + R_3 + R_4 & -R_4 \\ 0 & -R_4 + \alpha R_4 & R_4 + R_5 - \alpha R_4 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} E_1 - E_2 \\ E_2 - E_3 \\ 0 \end{pmatrix}$$

b) $I_1 = 1.3 \text{ A}$; $I_2 = -0.6 \text{ A}$; $I_3 = -1.2 \text{ A}$ **Solution 2**a) This is a difference amplifier. V_0 is given by

$$V_0 = -\left(\frac{R_3}{R_1 + R_2}\right)E_1 + \left(1 + \frac{R_3}{R_1 + R_2}\right)V^-$$

$$V^- = V^+$$

$$V^+ = I_1 \frac{R_4 R_5}{R_4 + R_5}$$

$$V_0 = -\left(\frac{R_3}{R_1 + R_2}\right)E_1 + \left(1 + \frac{R_3}{R_1 + R_2}\right)\frac{R_4 R_5}{R_4 + R_5}I_1$$

b) $V_0 = -30.42 \text{ V}$

$$c) I_{R5} = I_1 \frac{R_4}{R_4 + R_5} = 1.25 \text{ A}$$

Solution 3

$$v(t) = v(0)e^{-t/\tau} = 1e^{-2} = 0.14 \text{ V}$$

$$\tau = RC = 0.1 \text{ s}$$

$$t = 200 \text{ ms}$$