


Messina, 15 June 2022

**Exercise 1**

Solve the given circuit below by using the mesh analysis for the three currents as indicated.

a) Write the R matrix in analytical form.

b) Compute the value of the mesh currents  $J_1$ ,  $J_2$  and  $J_3$  (clockwise sense) using the following values for  $R_1 = 4 \Omega$ ,  $R_2 = 6 \Omega$ ,  $R_3 = 4 \Omega$ ,  $R_4 = 8 \Omega$ ,  $R_5 = 4 \Omega$ ,  $E_1 = 2 \text{ V}$ ,  $E_2 = 5 \text{ V}$ ,  $E_3 = 4 \text{ V}$ , and  $\alpha = -2 \Omega$ ; [ $J_1 \rightarrow \text{C-B-D-C}$ ;  $J_2 \rightarrow \text{C-A-B-C}$ ;  $J_3 \rightarrow \text{A-D-B-A}$ ]

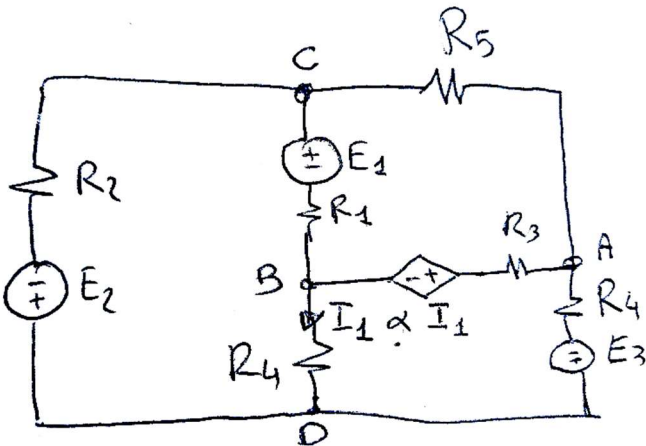


**Exercise 2**

Solve the given circuit below.

a) Compute analytically the expression of the  $V_0$  (help use the Millman theorem)

b) Compute the value of  $V_0$  considering the following parameters  $R_1 = 1 \Omega$ ,  $R_2 = 1 \Omega$ ,  $R_3 = 5 \Omega$ ,  $R_4 = 2 \Omega$ ,  $\alpha = 1$ ,  $E_1 = 10 \text{ V}$  and  $E_2 = -5 \text{ V}$ .

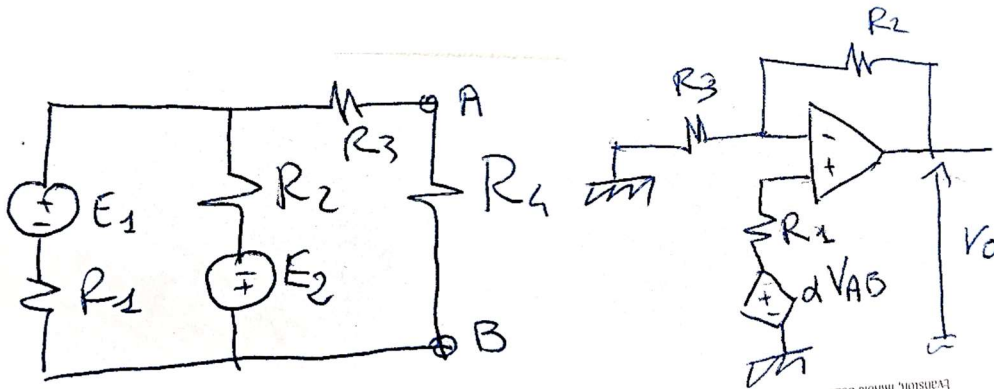

**Exercise 3**

a) For a given an RL circuit with  $R=2\Omega$  and  $L=0.5 \text{ H}$ . Compute the current flowing into the inductor  $L$  after 100 ms  $i_L(100 \text{ ms})$  considering that the current at  $t=0\text{s}$  flowing into the inductor is equal to 1A ( $i_L(0)=1\text{A}$ ).

Sign here \_\_\_\_\_

Exercise 1:

a)

b)

Exercise 2:

a)

b)

Exercise 3:

a)

### Solution 1

a)

$$\begin{pmatrix} R_1 + R_2 + R_4 & -R_1 & -R_4 \\ -R_1 & R_1 + R_3 + R_5 & -R_3 \\ -R_4 & -R_3 & 2R_4 + R_3 \end{pmatrix} \begin{pmatrix} J_1 \\ J_2 \\ J_3 \end{pmatrix} = \begin{pmatrix} -E_1 - E_2 \\ -\alpha I_1 + E_1 \\ \alpha I_1 + E_3 \end{pmatrix}$$

$$I_1 = J_1 - J_3$$

$$\begin{pmatrix} R_1 + R_2 + R_4 & -R_1 & -R_4 \\ -R_1 & R_1 + R_3 + R_5 & -R_3 \\ -R_4 & -R_3 & 2R_4 + R_3 \end{pmatrix} \begin{pmatrix} J_1 \\ J_2 \\ J_3 \end{pmatrix} = \begin{pmatrix} -E_1 - E_2 \\ -\alpha J_1 + \alpha J_3 + E_1 \\ \alpha J_1 - \alpha J_3 + E_3 \end{pmatrix}$$

$$\begin{pmatrix} R_1 + R_2 + R_4 & -R_1 & -R_4 \\ -R_1 + \alpha & R_1 + R_3 + R_5 & -R_3 - \alpha \\ -R_4 - \alpha & -R_3 & 2R_4 + R_3 + \alpha \end{pmatrix} \begin{pmatrix} J_1 \\ J_2 \\ J_3 \end{pmatrix} = \begin{pmatrix} -E_1 - E_2 \\ E_1 \\ E_3 \end{pmatrix}$$

b)  $J_1 = -0.31 \text{ A}$ ;  $J_2 = 0.08 \text{ A}$ ;  $J_3 = 0.14 \text{ A}$

### Solution 2

a) First of all we need to evaluate the  $V_{AB}$ . I will apply the Millman theorem and the voltage divider over the resistance  $R_3$  and  $R_4$ . The voltage  $V_{AB}$  is given by

$$V_{AB} = \left( \frac{E_1 / R_1 - E_2 / R_2}{1 / R_1 + 1 / R_2 + 1 / (R_3 + R_4)} \right) \frac{R_4}{R_3 + R_4}$$

The circuit with the OP AMP is a noninverting amplifier then we have

$$V_0 = \alpha V_{AB} \left( 1 + \frac{R_2}{R_3} \right)$$

$V_0$  is given by

b)  $V_0 = 2.4 \text{ V}$

### Solution 3

$$\tau = R / L = 4s$$

$$t = 100ms$$

$$i_L(t) = i_L(0)e^{-t/\tau} = 1e^{-0.1/4} = 0.98V$$