


Messina, 29 June 2022

Exercise 1

Solve the given circuit below by using the node analysis considering D as a reference node.

a) Write the G matrix in analytical form.

b) Compute the value of the nodal voltage V_A , V_B and V_C using the following values for $R_1 = 1 \Omega$, $R_2 = 4 \Omega$, $R_3 = 2 \Omega$, $R_4 = 2 \Omega$, $I_1 = 2 \text{ A}$, $I_2 = 1 \text{ A}$, $I_3 = 4 \text{ A}$, and $\alpha = 4 \Omega$; [Help: Consider the equivalence between voltage and current generators before to apply the node analysis]

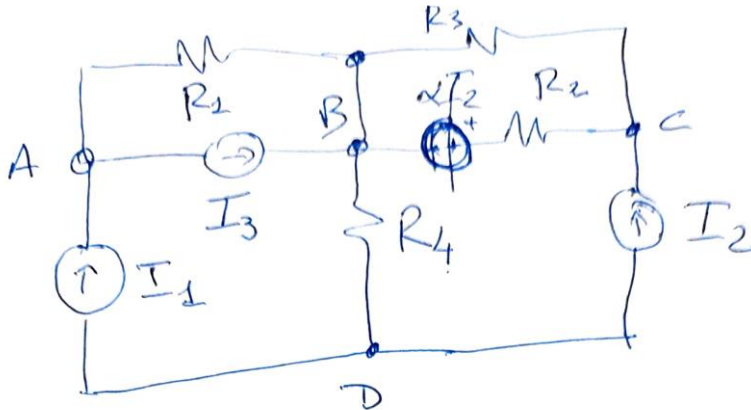


Exercise 2

Solve the given circuit below.

a) Compute analytically the expression of the V_A , V_B and V_0 .

b) Compute the value of V_0 considering the following parameters $R_1 = 1 \Omega$, $R_2 = 2 \Omega$, $R_3 = 4 \Omega$, $R_4 = 6 \Omega$, $R_5 = 100 \Omega$, $R_6 = 8 \Omega$, $R_7 = 9 \Omega$, $R_8 = 12 \Omega$, $R_9 = 5 \Omega$, $R_{10} = 10 \Omega$, $E_1 = 2 \text{ V}$, and $E_2 = -3 \text{ V}$.

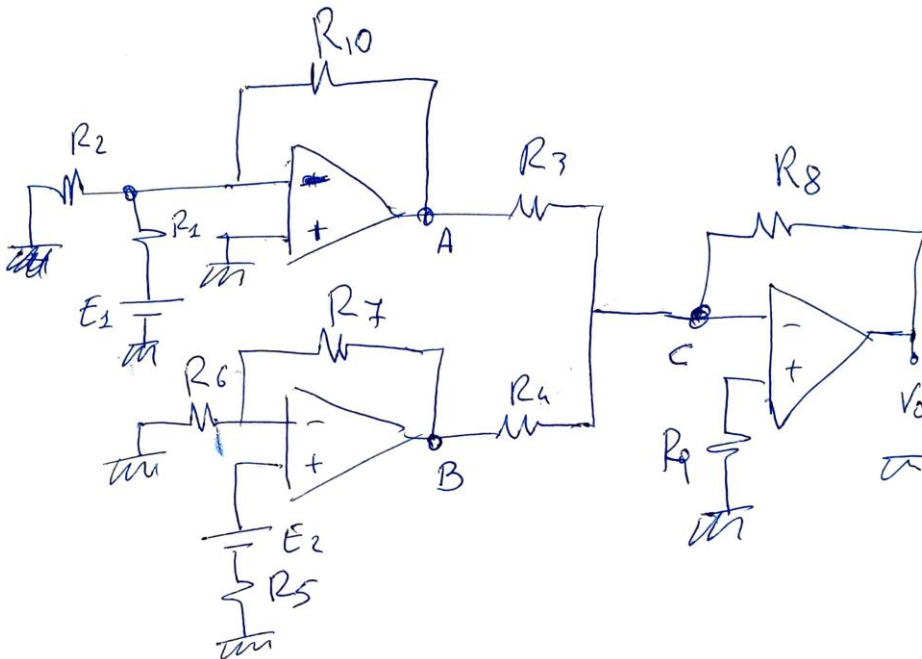

Exercise 3

a) For a given an RL circuit with $R=0.5\text{m}\Omega$ and $L=0.5 \text{ H}$. Compute the current flowing into the inductor L after $200 \mu\text{ s}$ $i_L(200 \mu\text{ s})$ considering that the current at $t=0\text{ s}$ flowing into the inductor is equal to 1A ($i_L(0)=5\text{ A}$).

Sign here _____

Exercise 1:

a)

b)

Exercise 2:

a)

b)

Exercise 3:

a)

Solution 1

a) Considering the equivalence between current and voltage generators, we have that the branch with the controlled voltage generator and the resistance R_2 in series are equivalent to a controlled current generator with a coefficient equal to α/R_2 with in parallel the same resistance R_2 . Mind that the term is with the current generator is a know value.

$$\begin{pmatrix} G_1 & -G_1 & 0 \\ -G_1 & G_1 + G_2 + G_3 + G_4 & -G_2 - G_3 \\ 0 & -G_2 - G_3 & G_2 + G_3 \end{pmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix} = \begin{pmatrix} I_1 - I_3 \\ I_3 - \alpha G_2 I_2 \\ \alpha G_2 I_2 + I_2 \end{pmatrix}$$

b) $V_A = 4 \text{ V}; V_B = 6 \text{ V}; V_C = 8.667\text{V}$

Solution 2

a) The voltage V_A, V_B and V_0 are given by

$$V_A = \left(\frac{E_1 R_2}{R_1 + R_2} \right) \frac{-R_{10}}{(R_{10} + R_1 R_2 / (R_1 + R_2))} \text{ (inverting amplifier); } V_B = E_2 \left(1 + \frac{R_7}{R_6} \right) \text{ (noninverting amplifier);}$$

$$V_0 = V_A \left(-\frac{R_8}{R_3} \right) + V_B \left(-\frac{R_8}{R_4} \right) \text{ (inverting amplifier where you add the inputs).}$$

b) $V_A = -1.25 \text{ V}; V_B = -5.25 \text{ V}; V_0 = 14.25 \text{ V};$

Solution 3

$$\tau = R / L = 0.1\text{ms}$$

$$t = 200\mu\text{s}$$

$$i_L(t) = i_L(0)e^{-t/\tau} = 4.0937\text{V}$$